

ELEC 374 – Digital Systems Engineering

Lab 1 Report

Divaydeep Singh, 20143859

Lucas Austin, 20061953

ALU

```
module alu(  
    input [3:0] select,  
    input clk,  
    input signed [31:0] A,  
    input signed [31:0] B,  
    output [63:0] Z,  
    output carry  
);  
  
wire [63:0] mult_res;  
wire[31:0] ror_res, rol_res;  
reg [31:0] RLo, RHi;  
assign Z = {RHi, RLo};  
initial RHi = 0;  
  
multiply mult(mult_res,A,B);  
rotate_right ror(ror_res,A,B);  
rotate_left rol(rol_res,A,B);  
  
always @ (posedge clk)  
begin  
    case(select)  
        4'b0001:  
            RLo <= A+B;  
        4'b0010:  
            RLo <= A-B;  
        4'b0011:  
            begin  
                RLo <= mult_res[31:0];  
                RHi <= mult_res[63:32];  
            end  
  
        4'b0101:  
            begin  
                RHi <= A%B;  
                RLo <= (A-RHi)/B;  
            end  
  
        4'b0110:  
            RLo <= A & B;  
        4'b0111:  
            RLo <= A|B;  
        4'b1000:  
            RLo <= ~B+1;  
        4'b1010:  
            RLo <= ~B;  
        4'b1011:  
            RLo <= A>>>B;  
        4'b1100:  
            RLo <= A<<B;  
        4'b1101:  
            RLo <= A>>B;  
        4'b1110:  
            RLo <= rol_res;  
        4'b1111:  
            RLo <= ror_res;  
        default:  
            RLo <= RLo;  
    endcase  
end  
endmodule
```

BUS

```
module bus(  
    input [31:0] busInR0, busInR1, busInR2, busInR3, busInR4, busInR5, busInR6, busInR7, busInR8, busInR9, busInR10, busInR11,  
        busInR12, busInR13, busInR14, busInR15, busInHI, busInLO, busInZ, busInPC, busInMDR, busInInPort, busInC,  
    input R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12out, R13out, R14out, R15out, HIout,  
        LOout, ZHighout, ZLowout, PCout, MDRout, InPortout, Cout,  
    output [31:0] bus,  
    input clk  
);  
  
wire[4:0] intermediate;  
  
bus_enc encoder(R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12out, R13out, R14out,  
    R15out, HIout, LOout, ZHighout, ZLowout, PCout, MDRout, InPortout, Cout, intermediate, clk);  
  
bus_mux multiplexer(busInR0, busInR1, busInR2, busInR3, busInR4, busInR5, busInR6, busInR7, busInR8, busInR9, busInR10, busInR11,  
    busInR12, busInR13, busInR14, busInR15, busInHI, busInLO, busInZ, busInPC, busInMDR, busInInPort, busInC,  
    intermediate, bus, clk);  
  
endmodule
```

BUS Encoder

```
module bus_enc(  
    input R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12out, R13out, R14out, R15out, HIout,  
        LOout, ZHighout, ZLowout, PCout, MDRout, InPortout, Cout,  
    output reg[4:0] encoded,  
    input clk  
);  
  
wire[31:0] outCombined;  
  
assign outCombined = {R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12out, R13out, R14out, R15out, HIout,  
    LOout, ZHighout, ZLowout, PCout, MDRout, InPortout, Cout};  
  
always @ (outCombined, clk)  
    case (outCombined)  
        32'b00000000000000000000000000000001 : encoded<=0;  
        32'b00000000000000000000000000000010 : encoded<=1;  
        32'b000000000000000000000000000000100 : encoded<=2;  
        32'b0000000000000000000000000000001000 : encoded<=3;  
        32'b00000000000000000000000000000010000 : encoded<=4;  
        32'b000000000000000000000000000000100000 : encoded<=5;  
        32'b0000000000000000000000000000001000000 : encoded<=6;  
        32'b00000000000000000000000000000010000000 : encoded<=7;  
        32'b000000000000000000000000000000100000000 : encoded<=8;  
        32'b0000000000000000000000000000001000000000 : encoded<=9;  
        32'b00000000000000000000000000000010000000000 : encoded<=10;  
        32'b000000000000000000000000000000100000000000 : encoded<=11;  
        32'b0000000000000000000000000000001000000000000 : encoded<=12;  
        32'b00000000000000000000000000000010000000000000 : encoded<=13;  
        32'b000000000000000000000000000000100000000000000 : encoded<=14;  
        32'b0000000000000000000000000000001000000000000000 : encoded<=15;  
        32'b00000000000000000000000000000010000000000000000 : encoded<=16;  
        32'b000000000000000000000000000000100000000000000000 : encoded<=17;  
        32'b0000000000000000000000000000001000000000000000000 : encoded<=18;  
        32'b00000000000000000000000000000010000000000000000000 : encoded<=19;  
        32'b000000000000000000000000000000100000000000000000000 : encoded<=20;  
        32'b0000000000000000000000000000001000000000000000000000 : encoded<=21;  
        32'b00000000000000000000000000000010000000000000000000000 : encoded<=22;  
        32'b000000000000000000000000000000100000000000000000000000 : encoded<=23;  
        default : encoded<=5'bx;  
    endcase
```

BUS Multiplexer

```
module bus_mux(  
    input [31:0] busInR0, busInR1, busInR2, busInR3, busInR4, busInR5, busInR6, busInR7, busInR8, busInR9, busInR10, busInR11,  
            busInR12, busInR13, busInR14, busInR15, busInHI, busInLO, busInZ, busInPC, busInMDR, busInInPort, busInC,  
    input [4:0] encoded,  
    output reg [31:0] bus,  
    input clk  
);  
  
    always @ (encoded, clk)  
        case (encoded)  
            23 : bus<=busInR0;  
            22 : bus<=busInR1;  
            21 : bus<=busInR2;  
            20 : bus<=busInR3;  
            19 : bus<=busInR4;  
            18 : bus<=busInR5;  
            17 : bus<=busInR6;  
            16 : bus<=busInR7;  
            15 : bus<=busInR8;  
            14 : bus<=busInR9;  
            13 : bus<=busInR10;  
            12 : bus<=busInR11;  
            11 : bus<=busInR12;  
            10 : bus<=busInR13;  
            9 : bus<=busInR14;  
            8 : bus<=busInR15;  
            7 : bus<=busInHI;  
            6 : bus<=busInLO;  
            5 : bus<=busInZ;  
            4 : bus<=busInZ;  
            3 : bus<=busInPC;  
            2 : bus<=busInMDR;  
            1 : bus<=busInInPort;  
            0 : bus<=busInC;  
            default : bus<=31'bx;  
        endcase  
  
endmodule
```

General Register

```
module gen_reg(  
    output reg[31:0] Q,  
    input [31:0] D,  
    input en, clr, clk  
);  
  
    initial Q = 0;  
  
    always @(posedge clk)  
        begin  
            if(clr)  
                Q = 0;  
            else if(en)  
                Q = D;  
        end  
endmodule
```

DataPath

```
module main1(
    input R0in, R1in, R2in, R3in, R4in, R5in, R6in, R7in, R8in, R9in, R10in, R11in, R12in, R13in, R14in, R15in,
    input R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12out, R13out, R14out, R15out,
    input HIin, LOin, PCin, IRin, Yin, InPortout, Zin,
    input HIout, LOout, PCout, MDRout, MDRin, MARin, MDRread, Cout, clk, IncPC, ZLowout, ZHighout,
    input [3:0] ALUselect,
    input [31:0] MDatain,

    output R0, R1, R2, R3, R4, R5, R6, R7, R8, R9, R10, R11, R12, R13, R14, R15,
    output [63:0] ZReg
);

wire[31:0] bus;
wire clr;
wire IROut;
wire [31:0] YData, XData;
wire [31:0] ZLowData, ZHighData;

wire [31:0] busInR0, busInR1, busInR2, busInR3, busInR4, busInR5, busInR6, busInR7, busInR8, busInR9, busInR10, busInR11, busInR12, busInR13, busInR14, busInR15, busInPC,
    busInMAR, busInMDR, busInHI, busInLO, busInZ, busInInPort, busInC;

gen_reg r0(busInR0, bus, R0in, clr, clk);
gen_reg r1(busInR1, bus, R1in, clr, clk);
gen_reg r2(busInR2, bus, R2in, clr, clk);
gen_reg r3(busInR3, bus, R3in, clr, clk);
gen_reg r4(busInR4, bus, R4in, clr, clk);
gen_reg r5(busInR5, bus, R5in, clr, clk);
gen_reg r6(busInR6, bus, R6in, clr, clk);
gen_reg r7(busInR7, bus, R7in, clr, clk);
gen_reg r8(busInR8, bus, R8in, clr, clk);
gen_reg r9(busInR9, bus, R9in, clr, clk);
gen_reg r10(busInR10, bus, R10in, clr, clk);
gen_reg r11(busInR11, bus, R11in, clr, clk);
gen_reg r12(busInR12, bus, R12in, clr, clk);
gen_reg r13(busInR13, bus, R13in, clr, clk);
gen_reg r14(busInR14, bus, R14in, clr, clk);
gen_reg r15(busInR15, bus, R15in, clr, clk);

gen_reg ir(IROut, bus, IRin, clr, clk);
pc_reg pc(busInPC, bus, PCin, IncPC, clr, clk);

gen_reg mar(busInMAR, bus, MARin, clr, clk);
mdr_reg mdr(busInMDR, MDatain, bus, MDRin, MDRread, clr, clk);

gen_reg hi(busInHI, bus, HIin, clr, clk);
gen_reg lo(busInLO, bus, LOin, clr, clk);
gen_reg y(YData, bus, Yin, clr, clk);
z_reg_64 z(busInZ, ZReg, Zin, ZLowout, ZHighout, clr, clk);

//ALU
//alu alu(ALUselect, YData, ZLowData, ZHighData, carry);
alu alu(ALUselect, clk, YData, bus, ZReg, carry);
//assign ZData = ZReg[63:0];
//assign busInZHI = ZReg[63:32];
//assign busInZLO = ZReg[31:0];
// Bus
bus bus_inst(busInR0, busInR1, busInR2, busInR3, busInR4, busInR5, busInR6, busInR7, busInR8, busInR9, busInR10, busInR11,
    busInR12, busInR13, busInR14, busInR15, busInHI, busInLO, busInZ, busInPC, busInMDR, busInInPort, busInPC,
    R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12out, R13out, R14out, R15out, HIout,
    LOout, ZHighout, ZLowout, PCout, MDRout, InPortout, Cout, bus, clk);
endmodule
```

Datapath Testbench

```
module datapath_tb;

    reg R0in, R1in, R2in, R3in, R4in, R5in, R6in, R7in, R8in, R9in, R10in, R11in, R12in, R13in, R14in, R15in;

    reg R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12out, R13out, R14out, R15out;

    reg HIin, LOin, PCin, IRin, Yin, InPortout, Zin;

    reg HIout, LOout, PCout, MDRout, MDRin, MARin, MDRread, Cout, clk, IncPC, ZLowout, ZHighout;

    reg[3:0] ALUselect;
    reg[31:0] MDatain;
    reg Read;

    wire R0, R1, R2, R3, R4, R5, R6, R7, R8, R9, R10, R11, R12, R13, R14, R15, HI, LO, IR, BusMuxOut;
    wire[63:0] ZReg;

    parameter Default = 4'b0000, Reg_load1a = 4'b0001, Reg_load1b = 4'b0010, Reg_load2a = 4'b0011, Reg_load2b = 4'b0100,
        Reg_load3a = 4'b0101, Reg_load3b = 4'b0110, T0 = 4'b0111, T1 = 4'b1000, T2 = 4'b1001, T3 = 4'b1010, T4 = 4'b1011,
        T5 = 4'b1100;

    reg[3:0] Present_state = Default;

    main1 DUT
        (.R0in(R0in), .R1in(R1in), .R2in(R2in), .R3in(R3in), .R4in(R4in), .R5in(R5in), .R6in(R6in), .R7in(R7in), .R8in(R8in), .R9in(R9in),
        .R10in(R10in), .R11in(R11in), .R12in(R12in), .R13in(R13in), .R14in(R14in), .R15in(R15in), .R0out(R0out), .R1out(R1out), .R2out(R2out),
        .R3out(R3out), .R4out(R4out), .R5out(R5out), .R6out(R6out), .R7out(R7out), .R8out(R8out), .R9out(R9out), .R10out(R10out), .R11out(R11out),
        .R12out(R12out), .R13out(R13out), .R14out(R14out), .R15out(R15out), .HIin(HIin), .LOin(LOin), .PCin(PCin), .IRin(IRin), .Yin(Yin), .InPortout(InPortout),
        .Zin(Zin), .HIout(HIout), .LOout(LOout), .PCout(PCout), .MDRout(MDRout), .MDRin(MDRin), .MARin(MARin), .MDRread(Read), .Cout(Cout), .clk(clk), .IncPC(IncPC),
        .ZLowout(ZLowout), .ZHighout(ZHighout), .ALUselect(ALUselect), .MDatain(MDatain), .R0(R0), .R1(R1), .R2(R2), .R3(R3), .R4(R4), .R5(R5), .R6(R6), .R7(R7), .R8(R8),
        .R9(R9), .R10(R10), .R11(R11), .R12(R12), .R13(R13), .R14(R14), .R15(R15), .ZReg(ZReg));

    initial
        begin
            clk = 0;
            forever #10 clk = ~clk;
        end
end
```

```

always @(posedge clk)
begin
    case(Present_state)
        Default      : #40 Present_state = Reg_load1a;
        Reg_load1a   : #40 Present_state = Reg_load1b;
        Reg_load1b   : #40 Present_state = Reg_load2a;
        Reg_load2a   : #40 Present_state = Reg_load2b;
        Reg_load2b   : #40 Present_state = Reg_load3a;
        Reg_load3a   : #40 Present_state = Reg_load3b;
        Reg_load3b   : #40 Present_state = T0;

        T0           : #60 Present_state = T1;
        T1           : #60 Present_state = T2;
        T2           : #60 Present_state = T3;
        T3           : #60 Present_state = T4;
        T4           : #60 Present_state = T5;
    endcase
end

always @(Present_state)
begin
    case(Present_state)
        Default:begin
            R0out <=0; R1out <=0; R2out <=0; R3out <=0; R4out <=0; R5out <=0; R6out <=0; R7out <=0;
            R8out <=0; R9out <=0; R10out <=0; R11out <=0; R12out <=0; R13out <=0; R14out <=0; R15out <=0;
            HIout <=0; LOout <=0; InPortout <=0; Cout <=0;
            PCout <=0; ZLowout <=0; ZHighout <=0; MDRout <=0;
            R2out <=0; R4out <=0; MARin <=0; Zin <=0;
            PCin <=0; MDRin <=0; IRin <=0; Yin <=0;
            IncPC <=0; Read <=0; ALUselect <=0;
            R5in <=0; R2in <=0; R4in <=0; MDatain <=32'h00000000;

        end
        Reg_load1a:begin
            Read = 0; MDRin = 0;
            MDatain <= 32'h00000002;
            #10 Read <= 1; MDRin <= 1;
            #15 Read <= 0; MDRin <= 0;
        end
        Reg_load1b: begin
            #10 MDRout <= 1; R2in <= 1;
            #15 MDRout <= 0; R2in <= 0; // initialize R2 with the value $22
        end
        Reg_load2a: begin
            MDatain <= 32'h00000024;
            #10 Read <= 1; MDRin <= 1;
            #15 Read <= 0; MDRin <= 0;
        end
        Reg_load2b: begin
            #10 MDRout <= 1; R4in <= 1;
            #15 MDRout <= 0; R4in <= 0; // initialize R4 with the value $24
        end
        Reg_load3a: begin
            MDatain <= 32'h00000026;
            #10 Read <= 1; MDRin <= 1;
            #15 Read <= 0; MDRin <= 0;
        end
        Reg_load3b: begin
            #10 MDRout <= 1; R5in <= 1;
            #15 MDRout <= 0; R5in <= 0; // initialize R5 with the value $26
        end
        T0: begin // see if you need to de-assert these signals
            PCout <= 1; MARin <= 1; IncPC <= 1; Zin <= 1;
        end
        T1: begin
            PCout <= 0; MARin <= 0; IncPC <= 0; Zin <= 0;
            ZLowout <= 1; PCin <= 1; Read <= 1; MDRin <= 1;
            MDatain <= 32'h4A920000; // opcode for "and R5, R2, R4"
            //MDatain <= 32'h52920000; // opcode for "or R5, R2, R4"
            //MDatain <= 32'h1A920000; // opcode for "add R5, R2, R4"
            //MDatain <= 32'h22920000; // opcode for "sub R5, R2, R4"
            //MDatain <= 32'h71200000; // opcode for "mul R2, R4"
            //MDatain <= 32'h79200000; // opcode for "div R2, R4"
            //MDatain <= 32'h2A920000; // opcode for "shr R5, R2, R4"
            //MDatain <= 32'h32920000; // opcode for "shl R5, R2, R4"
            //MDatain <= 32'h3A920000; // opcode for "ror R5, R2, R4"
            //MDatain <= 32'h42920000; // opcode for "rol R5, R2, R4"
            //MDatain <= 32'h81200000; // opcode for "neg R2, R4"
            //MDatain <= 32'h89200000; // opcode for "div R2, R4"
        end
        T2: begin
            ZLowout <= 0; PCin <= 0; Read <= 0; MDRin <= 0;
            MDRout <= 1; IRin <= 1;
        end
        T3: begin
            MDRout <= 0; IRin <= 0;
            R2out <= 1; Yin <= 1;
        end
        T4: begin
            Yin <=0; R2out <= 0; R4out <= 1; ALUselect <= 4'b0110; Zin <= 1;
        end
        T5: begin
            ALUselect <= 4'b0000;
            R4out <= 0; Zin <=0; ZLowout <= 1; R5in <= 1;
        end
    endcase
end
endmodule

```

MDR register

```
module mdr_reg(out, MdataIn, bus, en, rd, clr, clk);
output reg [31:0] out;
input [31:0] MdataIn, bus;
input en, rd, clr, clk;
wire [31:0] in;
always @(posedge clk)
    if(clr)
        out=0;
    else if(en)
        if(rd)
            out = MdataIn;
        else
            out = bus;
endmodule
```

Multiplication Algorithm

```
module multiply(
    output[63:0] p,
    input signed [31:0] x,y
);

    reg[2:0] cc[(32/2)-1:0];
    reg[32:0] pp[(32/2)-1:0];
    reg[63:0] spp[(32/2)-1:0];
    reg[63:0] prod;
    wire[32:0] inv_x;
    integer kk,i;

    assign inv_x = {~x[31], ~x}+1;

    always @(x or y or inv_x)
    begin
        cc[0] = {y[1],y[0],1'b0};

        for(kk=1;kk<(32/2);kk=kk+1)
            cc[kk] = {y[2*kk+1],y[2*kk],y[2*kk-1]};
        for(kk=0;kk<(32/2);kk=kk+1)
            begin
                case(cc[kk])
                    3'b001,3'b010:pp[kk]={x[32-1],x};
                    3'b011:pp[kk]={x,1'b0};
                    3'b100:pp[kk]={inv_x[32-1:0],1'b0};
                    3'b101,3'b110:pp[kk] = inv_x;
                    default:pp[kk]=0;
                endcase
                spp[kk]=$signed(pp[kk]);
                for(i=0;i<kk;i=i+1)
                    spp[kk]={spp[kk],2'b00};
                end
                prod=spp[0];
                for(kk=1;kk<(32/2);kk=kk+1)
                    prod=prod+spp[kk];
                end
                assign p = prod;
            end
    endmodule
```

PC Reg

```
module pc_reg(
    output reg [31:0] Q,
    input [31:0] D,
    input wr, inc, clr, clk
);
    initial Q=0;
always @(posedge clk)
    begin
        if(clr)
            Q = 0;
        else if(wr)
            Q = D;
        else if(inc)
            Q = Q+1;
    end
endmodule
```

Rotate Register

```
module rotate_right(
    output [31:0] R,
    input [31:0] A, B
);
    wire [4:0] N;
    assign N = A % 32;
    assign R = (N == 31) ? {B[30:0], B[31:31]} :

        (N == 30) ? {B[29:0], B[31:30]} :
        (N == 29) ? {B[28:0], B[31:29]} :
        (N == 28) ? {B[27:0], B[31:28]} :
        (N == 27) ? {B[26:0], B[31:27]} :
        (N == 26) ? {B[25:0], B[31:26]} :
        (N == 25) ? {B[24:0], B[31:25]} :
        (N == 24) ? {B[23:0], B[31:24]} :
        (N == 23) ? {B[22:0], B[31:23]} :
        (N == 22) ? {B[21:0], B[31:22]} :
        (N == 21) ? {B[20:0], B[31:21]} :
        (N == 20) ? {B[19:0], B[31:20]} :
        (N == 19) ? {B[18:0], B[31:19]} :
        (N == 18) ? {B[17:0], B[31:18]} :
        (N == 17) ? {B[16:0], B[31:17]} :
        (N == 16) ? {B[15:0], B[31:16]} :
        (N == 15) ? {B[14:0], B[31:15]} :
        (N == 14) ? {B[13:0], B[31:14]} :
        (N == 13) ? {B[12:0], B[31:13]} :
        (N == 12) ? {B[11:0], B[31:12]} :
        (N == 11) ? {B[10:0], B[31:11]} :
        (N == 10) ? {B[9:0], B[31:10]} :
        (N == 9) ? {B[8:0], B[31:9]} :
        (N == 8) ? {B[7:0], B[31:8]} :
        (N == 7) ? {B[6:0], B[31:7]} :
        (N == 6) ? {B[5:0], B[31:6]} :
        (N == 5) ? {B[4:0], B[31:5]} :
        (N == 4) ? {B[3:0], B[31:4]} :
        (N == 3) ? {B[2:0], B[31:3]} :
        (N == 2) ? {B[1:0], B[31:2]} :
        (N == 1) ? {B[0:0], B[31:1]} :
        B[31:0];
endmodule
```



```

module rotate_left(
    output [31:0] R,
    input [31:0] A, B
);

    wire [4:0] N;
    assign N = A % 32;
    assign R = (N == 31) ? {B[0:0], B[31:1]} :
        (N == 30) ? {B[1:0], B[31:2]} :
        (N == 29) ? {B[2:0], B[31:3]} :
        (N == 28) ? {B[3:0], B[31:4]} :
        (N == 27) ? {B[4:0], B[31:5]} :
        (N == 26) ? {B[5:0], B[31:6]} :
        (N == 25) ? {B[6:0], B[31:7]} :
        (N == 24) ? {B[7:0], B[31:8]} :
        (N == 23) ? {B[8:0], B[31:9]} :
        (N == 22) ? {B[9:0], B[31:10]} :
        (N == 21) ? {B[10:0], B[31:11]} :
        (N == 20) ? {B[11:0], B[31:12]} :
        (N == 19) ? {B[12:0], B[31:13]} :
        (N == 18) ? {B[13:0], B[31:14]} :
        (N == 17) ? {B[14:0], B[31:15]} :
        (N == 16) ? {B[15:0], B[31:16]} :
        (N == 15) ? {B[16:0], B[31:17]} :
        (N == 14) ? {B[17:0], B[31:18]} :
        (N == 13) ? {B[18:0], B[31:19]} :
        (N == 12) ? {B[19:0], B[31:20]} :
        (N == 11) ? {B[20:0], B[31:21]} :
        (N == 10) ? {B[21:0], B[31:22]} :
        (N == 9) ? {B[22:0], B[31:23]} :
        (N == 8) ? {B[23:0], B[31:24]} :
        (N == 7) ? {B[24:0], B[31:25]} :
        (N == 6) ? {B[25:0], B[31:26]} :
        (N == 5) ? {B[26:0], B[31:27]} :
        (N == 4) ? {B[27:0], B[31:28]} :
        (N == 3) ? {B[28:0], B[31:29]} :
        (N == 2) ? {B[29:0], B[31:30]} :
        (N == 1) ? {B[30:0], B[31:31]} :
        B[31:0];

endmodule

```

Z_Register

```


module z_reg_64 (
    output reg [31:0] Z,
    input [63:0] D,
    input ZIn, ZLowOut, ZHighOut, clr, clk
);

    reg[63:0] ZData;


    always @(clk, D)
        begin
            if(clr)
                begin
                    Z<=64'h0000000000000000;
                end
            else if(ZIn)
                begin
                    ZData<=D;
                end
            if(ZLowOut)
                begin
                    Z<=ZData[31:0];
                end
            else if(ZHighOut)
                begin
                    Z<=ZData[63:32];
                end
        end
    end
endmodule

```


Waveform Part 3a

 

Waveform Part 3b

 

Waveform Part 3c

 

Waveform Part 3d

